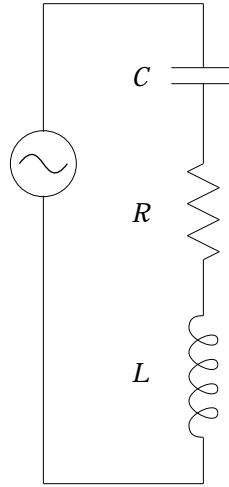




The LCR circuit

$$\mathcal{E}(t) = \mathcal{E}_m \sin(\omega t)$$



$$i(t) = I(\omega) \sin(\omega t - \phi(\omega))$$

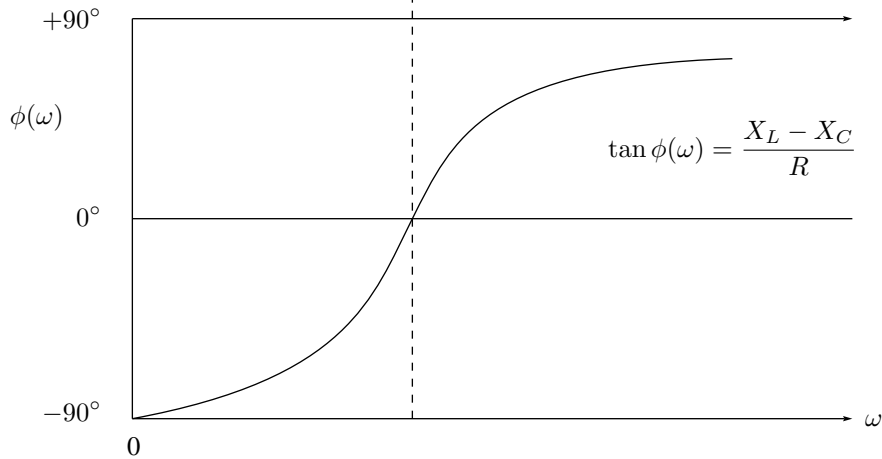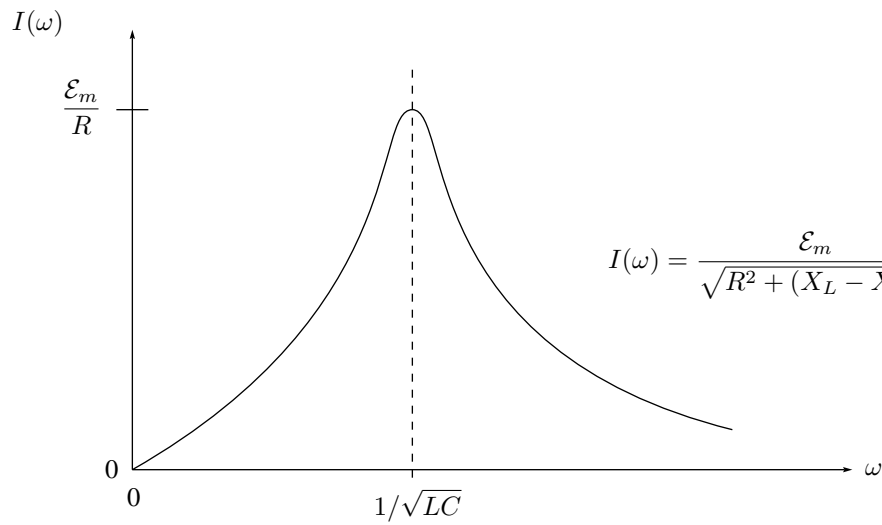define reactance: $X_C = \frac{1}{\omega C}$; $X_L = \omega L$



Slow changes ($\omega \ll 1/\sqrt{LC}$)

- capacitive reactance dominates $\Rightarrow I(\omega)$ small
- $v_C(t) \approx \mathcal{E}(t)$
- $\frac{q(t)}{C} \approx \mathcal{E}_m \sin(\omega t)$
- $i(t) = \frac{dq(t)}{dt} \approx C\mathcal{E}_m\omega \cos(\omega t)$
- c.f. $i(t) = I \sin(\omega t - \phi) \Rightarrow \phi \approx -90^\circ$

Fast changes ($\omega \gg 1/\sqrt{LC}$)

- inductive reactance dominates $\Rightarrow I(\omega)$ small
- $v_L(t) \approx \mathcal{E}(t)$
- $L \frac{di(t)}{dt} \approx \mathcal{E}_m \sin(\omega t)$
- $i(t) = \int \frac{di(t)}{dt} dt \approx -\frac{\mathcal{E}_m}{\omega L} \cos(\omega t)$
- c.f. $i(t) = I \sin(\omega t - \phi) \Rightarrow \phi \approx +90^\circ$

At resonance ($\omega = 1/\sqrt{LC}$)

- $v_C(t)$ and $v_L(t)$ can both be quite large, but
- $v_C(t) = -v_L(t)$ so $v_R(t) = \mathcal{E}(t)$
- $\Rightarrow I(\omega) = \mathcal{E}_m/R$ (a maximum)
- $\phi(\omega) = 0^\circ$