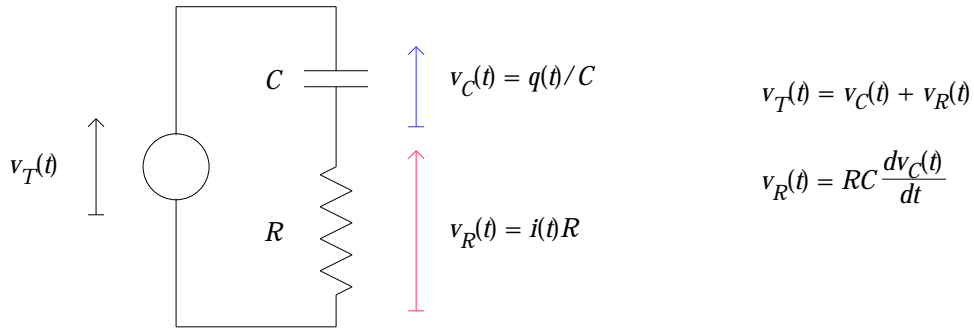


# RC circuit; slow changes



Slow changes (low frequency):  $T/2 \gg RC$ ;  $f \ll 1/(2RC)$

